

Logic and Computer Design Fundamentals

Midterm Review

Ming Cai

cm@zju.edu.cn

College of Computer Science and Technology,
Zhejiang University

Previous Year's Final Exam

1. Fill in the blank (20 points, 2pt/per)
2. Single Choice (20 points, 2pt/per)
3. Optimization (12 points, 6pt/per)
4. Circuit Analysis (18 points)
 - Combinational circuit
 - Sequential circuit
5. Logic Design (30 points)
 - Combinational circuit
 - Sequential circuit

Course Review

HIGHLIGHTS & PROBLEMS

Chapter 1

■ Conversion between number systems

- Binary number, hexadecimal number

- Eg. $(1101\ 1111)_2 = (DF)_{16}$

Decimal	Binary	Octal	Hexadecimal
369.3125	101110001.0101	561.24	171.5
189.625	10111101.101	275.5	BD.A
214.625	11010110.101	326.5	D6.A
62407.625	1111001111000111.101	171707.5	F3C7.A

■ Conversion between binary number and decimal code

- BCD (binary-coded decimal)

- Eg. $(1001\ 0101)_{BCD} \rightarrow (0101\ 1111)_2 \rightarrow (5F)_{16}$

- Parity Bit

- $100\ 0001 \rightarrow 0100\ 0001$ (with even parity) $\rightarrow 1100\ 0001$ (with odd parity)
- How to generate odd parity bit P for any 5-bit binary number $D_4D_3D_2D_1D_0$?

■ Gray Code & ASCII Character Code

Chapter 2

■ Boolean algebra

- DeMorgan's law: $\overline{(X + Y)} = \overline{X} \overline{Y}$ and $\overline{(XY)} = \overline{X} + \overline{Y}$
- Distributive laws: $X + YZ = (X + Y)(X + Z)$
- Dual of an algebraic expression: OR \longleftrightarrow AND, 0's \longleftrightarrow 1's
- Consensus theorem: $XY + \overline{X}Z + YZ = XY + \overline{X}Z$, $(X + Y)(\overline{X} + Z)(Y + Z) = (X + Y)(\overline{X} + Z)$

■ Complement of a function

- OR \longleftrightarrow AND, 0's \longleftrightarrow 1's, $X \longleftrightarrow \overline{X}$

■ Standard forms

- Minterms, Maxterms, Canonical forms (SOM, POM)
- Product terms, sum terms, SOP, POS
- Relationship between SOM and POM? SOM and SOP?

■ Two-level circuit optimization

- Cost criteria: gate input cost
- Karnaugh map (K-map), Prime Implicants, Essential Prime Implicants
- Simplifying in SOP form (with don't care conditions)

Chapter 2

- Other gates
 - NAND/NOR, XOR/XNOR, Odd/Even Function, Buffer, 3-state buffer
- Exclusive-OR operator and gates
 - Identities of XOR operation:
 - $X \oplus \overline{Y} = \overline{X} \oplus Y = \overline{(X \oplus Y)}$ $X \oplus \overline{(Y \oplus Z)} = \overline{(X \oplus Y)} \oplus Z = \overline{(X \oplus Y \oplus Z)}$
 - Odd function and even function
 - Use odd function to generate even parity bit
 - Use even function to generate odd parity bit
 - The even function is obtained by replacing the output gate with an XNOR gate. $P_{\text{odd}} = X \oplus Y \oplus Z$, $P_{\text{even}} = \overline{P_{\text{odd}}} = \overline{(X \oplus Y \oplus Z)}$
- High-impedance outputs
 - 3-state buffer
 - Transmission gates


EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

Chapter 2

■ Problems:

- The dual of an algebraic expression is obtained by 1) interchanging OR and AND operations and 2) replacing 1's by 0's and 0's by 1's.
- Use DeMorgan's Theorem to complement a function: 1) interchange AND and OR operators and 2) complement each constant value and literal
- Four variables odd function has C “1” squares in its corresponding K-Map.
A. 4 B. 7 C. 8 D. 14
- The gate input cost G of function $F = AB(C + D) + C(B\bar{D} + \bar{A}D)$ is A.
A. 15 B. 14 C. 13 D. 12
- Which of the following logical gates can be used as a controllable inverter? B.
A. AND gate B. XOR gate C. Buffer gate D. OR gate
- The Essential Prime Implicants in the K-Map given below are B.
A. $Y'Z'$, XZ' B. $X'Y'$, XY C. XY , XZ' D. $Y'Z'$, $X'Y'$
- Given below are the waveforms of input A, B and output F of a logic device. Then the device is a C gate.

A. NAND B. NOR C. XOR D. OR

 


				Y
	1	1		
	1		1	1
W	1		1	1
	1	1		
				Z

Chapter 2

■ Problems:

 1. According to the following logic circuit diagram, write down the corresponding Boolean function and optimize it to the form of SOP



2. Given a Boolean function


$$F(W, X, Y, Z) = \sum m(4, 6, 7, 8, 12, 15) + \sum d(2, 3, 5, 10, 11)$$

Optimize F together with the don't-care conditions d using a K-map

Chapter 3

■ Technology parameters

 - fan-in, fan-out, noise margin, cost, transition time, propagation delay, power dissipation




t_r = Rise transition time
 t_f = Fall transition time
 t_{phl} = Propagation delay high-low
 t_{plh} = Propagation delay low-high

- Delay Model: transport delay, inertial delay, rejection time
- How to calculate gate delay based on fan-out?

Chapter 3

- Methods of Describing Logic Events
 - Truth Table, Timing Diagram, Boolean Function, Karnaugh Maps, Logic Circuit
- Design procedure: specification, formulation, optimization, technology mapping, verification
 - Hierarchical Design
- Seven-segment display
 - How to design a BCD-to-Seven-Segment decoder? [example 3-2](#)
- Technology mapping
 - How to implement a Boolean function with NAND gates?

 


Chapter 3

- n-to-m-Line Decoder
 - n inputs and m outputs with $n \leq m \leq 2^n$
- m-to-n-Line Encoder
 - m inputs and n outputs with $n \leq m \leq 2^n$
- Multiplexer
 - n control inputs (selection inputs), m inputs and one output with $m < 2^n$
- Demultiplexer: Decoder with Enable
- Combinational Function Implementation
 - Decoders and OR gates,
 - Multiplexers
 - ROMs
 - PALs: doesn't provide full decoding of the variables, so it doesn't generate all the minterms
 - PLAs: similar to the PALs
 - Lookup Tables

Chapter 3


■ Combinational Function Implementation

- Any combinational circuit with n inputs and m outputs can be implemented with
 - an n -to- 2^n -line **decoder**, and m **OR** gates (one for each output)
- Implement m functions of n **variables** with
 - an m -wide 2^n -to-1-line **multiplexer**
- Implement m functions of $n+1$ variables with
 - an m -wide 2^n -to-1-line multiplexer and a single inverter

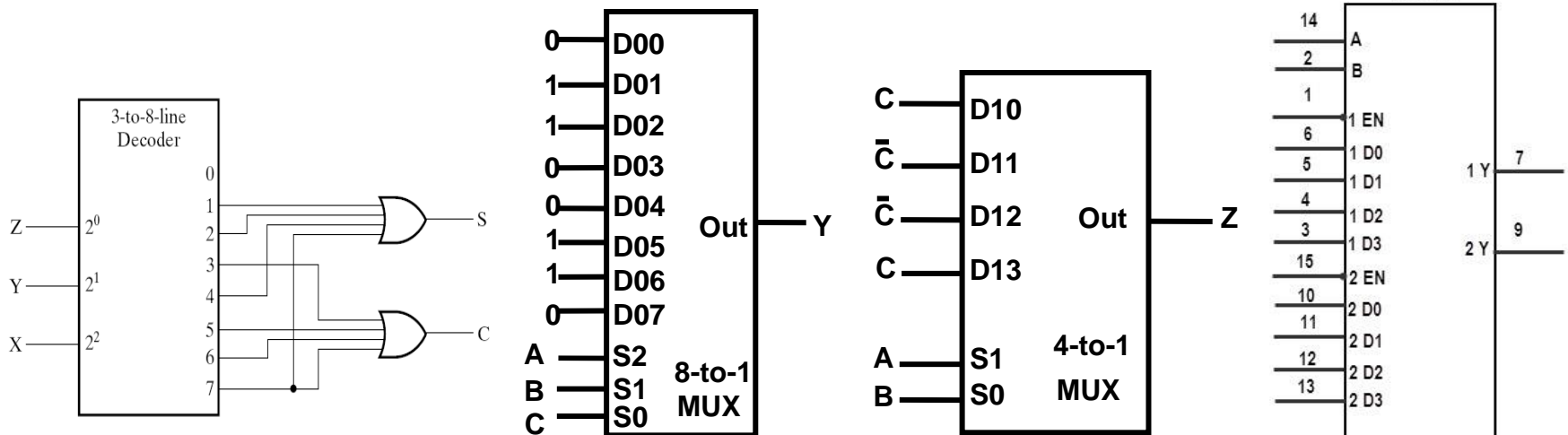


Chapter 3

- Problem: Design a 4-to-16 line decoder with **Enable** input using five 2-to-4 line decoders with **Enable** inputs.

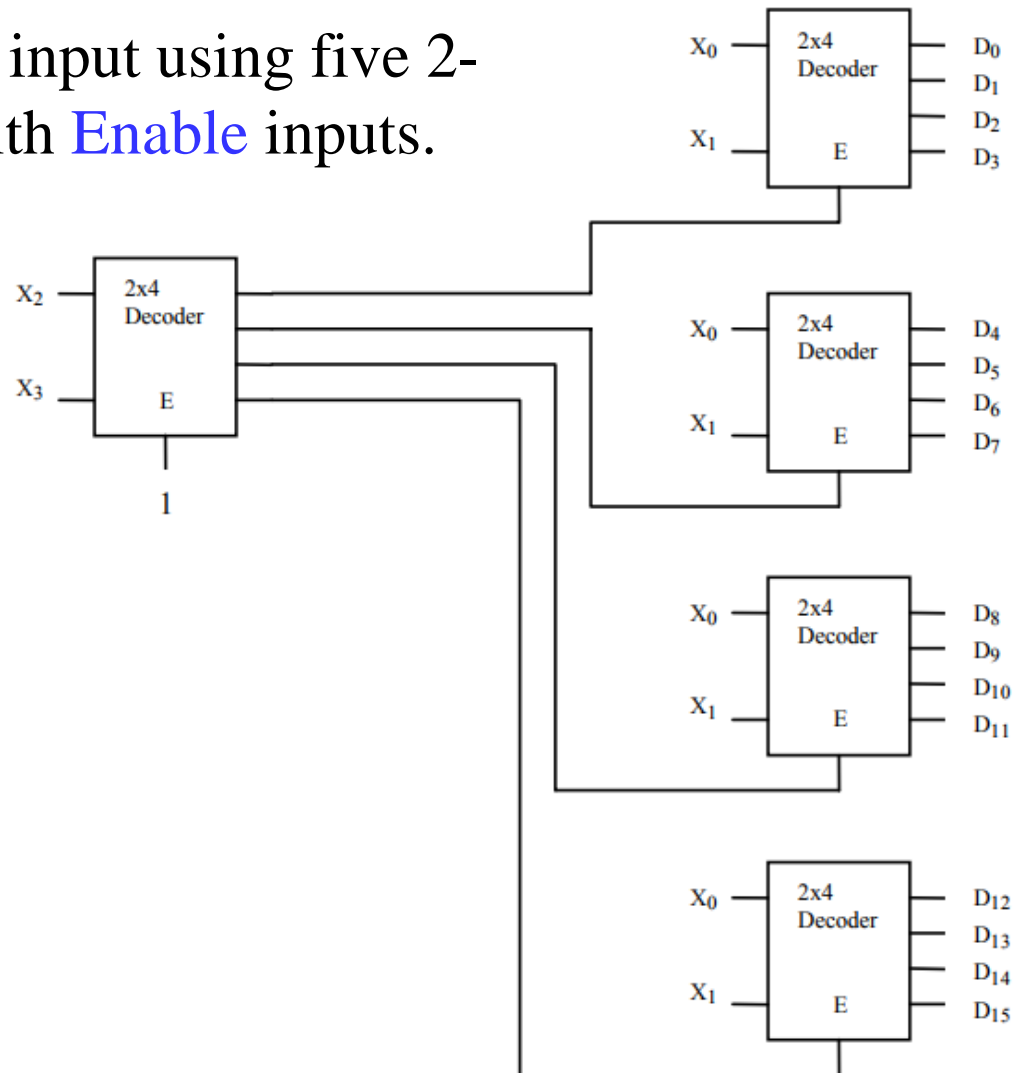

Chapter 3

 
- Problem: Give the canonical sum of product expression for the function which is implemented using the following circuit.



$$Y(A, B, C, D) = \Sigma_m(1, 2, 3, 6, 9, 10, 11, 13)$$

Chapter 3

 - Problem: Give the canonical sum of product expression for the function which is implemented using the following circuit.





- approach 2

$$\begin{aligned}
 Y &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C1 + \bar{A}B\bar{C}0 + \bar{A}BC\bar{D} + \\
 &\quad A\bar{B}\bar{C}D + A\bar{B}C1 + AB\bar{C}D + ABC0 \\
 &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \\
 &\quad A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD + AB\bar{C}D
 \end{aligned}$$

$$Y(A, B, C, D) = \Sigma_m(1, 2, 3, 6, 9, 10, 11, 13)$$

Chapter 3


- Half Adder
- Full Adder
 - *carry generate*: $X \cdot Y$
 - *carry propagate*: $X \oplus Y$
- Binary Ripple Carry Adder
- Carry Lookahead Adder
- Binary subtraction
 - Unsigned 2's Complement subtraction
 - Signed 2's Complement subtraction
 - $1100 - 0011 = 1001$
 - $0011 - 1100 = 0111$
- Signed-Complement Arithmetic
- Binary adder-subtractors

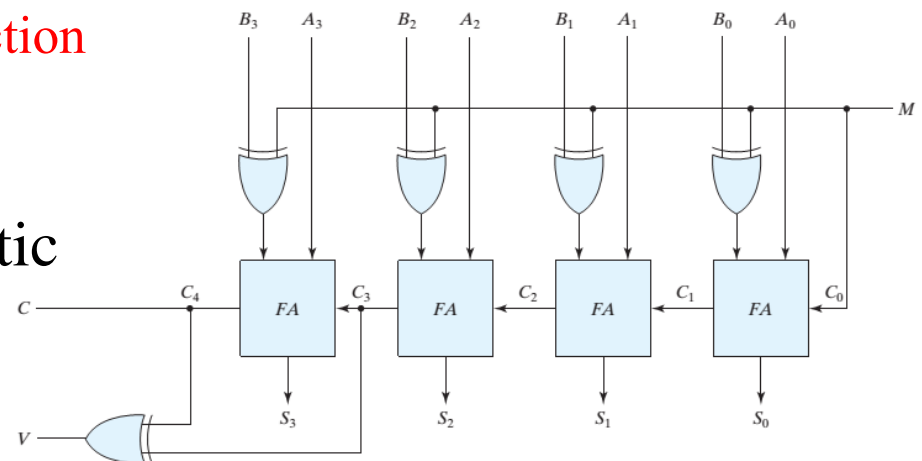 


Chapter 3

■ Design by Contraction

1. set $B = 001$  value fixing

 


2. simplifying the logic  contracting

 

Chapter 3

■ Arithmetic circuit design

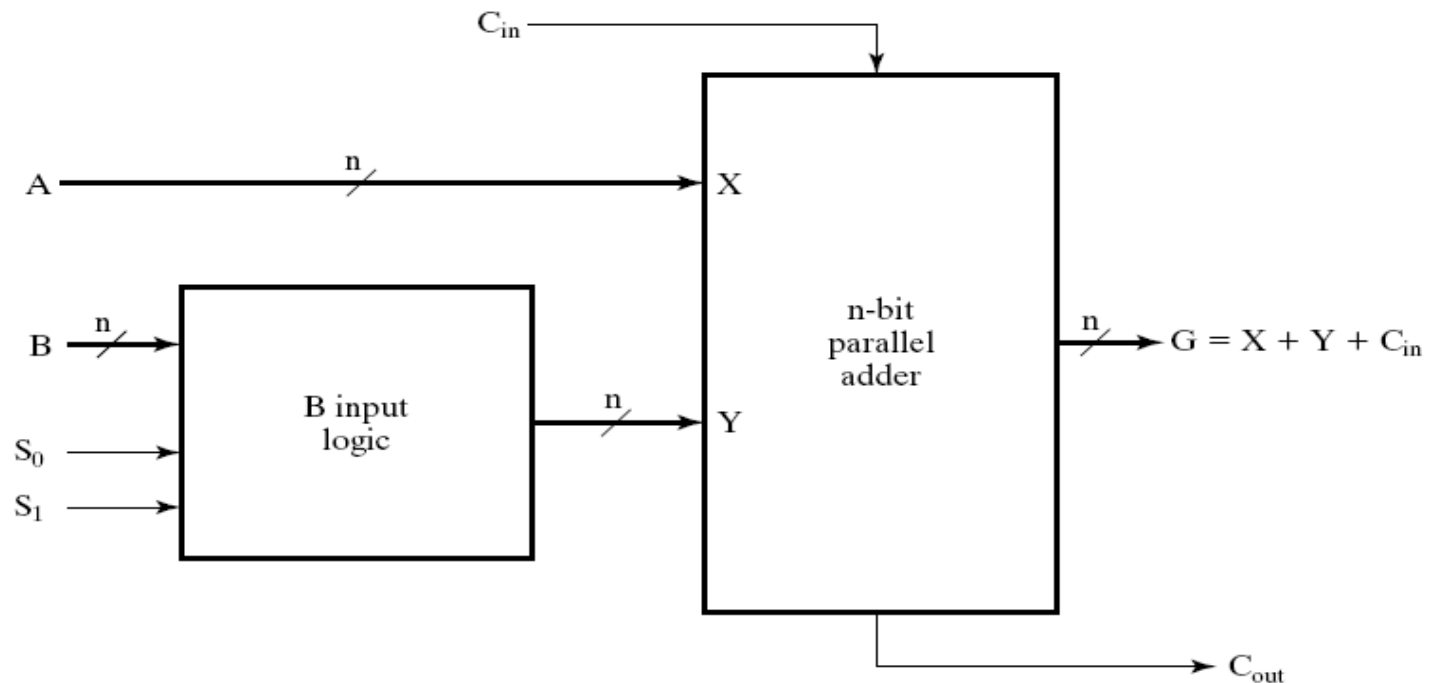


Select		Input	$G = A + Y + C_{in}$	
S_1	S_0	Y	$C_{in} \quad 0$	$C_{in} \quad 1$
0	0	all 0's	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	\overline{B}	$G = A + \overline{B}$	$G = A + \overline{B} + 1$ (subtract)
1	1	all 1's	$G = A - 1$ (decrement)	$G = A$ (transfer)

Chapter 3

- Problem: Implement a binary full adder with a **dual 4-to-1-line multiplexer** and a single inverter.

X	Y	C_{in}	S	C	
0	0	0	0	0	$S = C_{in}$
0	0	1	1	0	$C = 0$
0	1	0	1	0	$S = \overline{C_{in}}$
0	1	1	0	1	$C = C_{in}$
1	0	0	1	0	$S = \overline{C_{in}}$
1	0	1	0	1	$C = C_{in}$
1	1	0	0	1	$S = C_{in}$
1	1	1	1	1	$C = 1$

 



Chapter 3

- **Problem:** Using A Full Adder and logic gates to design a combinational circuit with three inputs, x, y, and z, and three outputs, A, B, and C.
- 1) When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input.
- 2) When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.

x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0


		y			
		\longleftrightarrow			
	$x \backslash yz$	00	01	11	10
	0			1	
x	1		1	1	1

$$A = xy + xz + yz$$

					
					
x\yz	00	01	11	10	
0		1		1	
1	1		1		

$$B = x \oplus y \oplus z$$

$$C = z'$$

 

Chapter 3

■ Problems



- Given a 4-bit full adder, design a 4-bit Incrementer-Decrementer circuit.

Inputs: $D = D_3D_2D_1D_0$ and S , Outputs: $Y = Y_3Y_2Y_1Y_0$ and C .

(1). When $S = 0$, circuit is an Incrementer: $Y = D + 1$. If $Y > 1111$, $C = 1$; other $C = 0$.

(2). When $S = 1$, circuit is a Decrementer: $Y = D - 1$. If $Y < 0000$, $C = 0$; other $C = 1$.

- Using a Full Adder and logic gates to design a combinational circuit that compares two 4-bit unsigned numbers A and B to see whether B is greater than A . The circuit has one output X , so that $X = 1$ if $A < B$ and $X = 0$ if $A \geq B$.

  


Chapter 5

- Programmable implementation technologies
 - PROM, PAL, PLA, FPGA

AND	OR	DEVICE
Fixed	Fixed	Not Programmable
Fixed	Programmable	PROM
Programmable	Fixed	PAL
Programmable	Programmable	PLA

Chapter 5

- Programmable implementation technologies
 - PROM
 - Can any combinational circuit with n inputs and m outputs be implemented with
 - a PROM with n inputs and m outputs ?
 - a PLA with n inputs and m outputs ?
 - a PAL with n inputs and m outputs ?

 

Chapter 5


■ Programmable implementation technologies

- PAL

$$W = \overline{\overline{A}}\overline{\overline{B}}C + \overline{A}BC$$

$$F1 = X = \overline{A}\overline{\overline{B}}\overline{\overline{C}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + W$$


$$F2 = Y = \overline{A}B + \overline{B}C + \overline{A}C$$

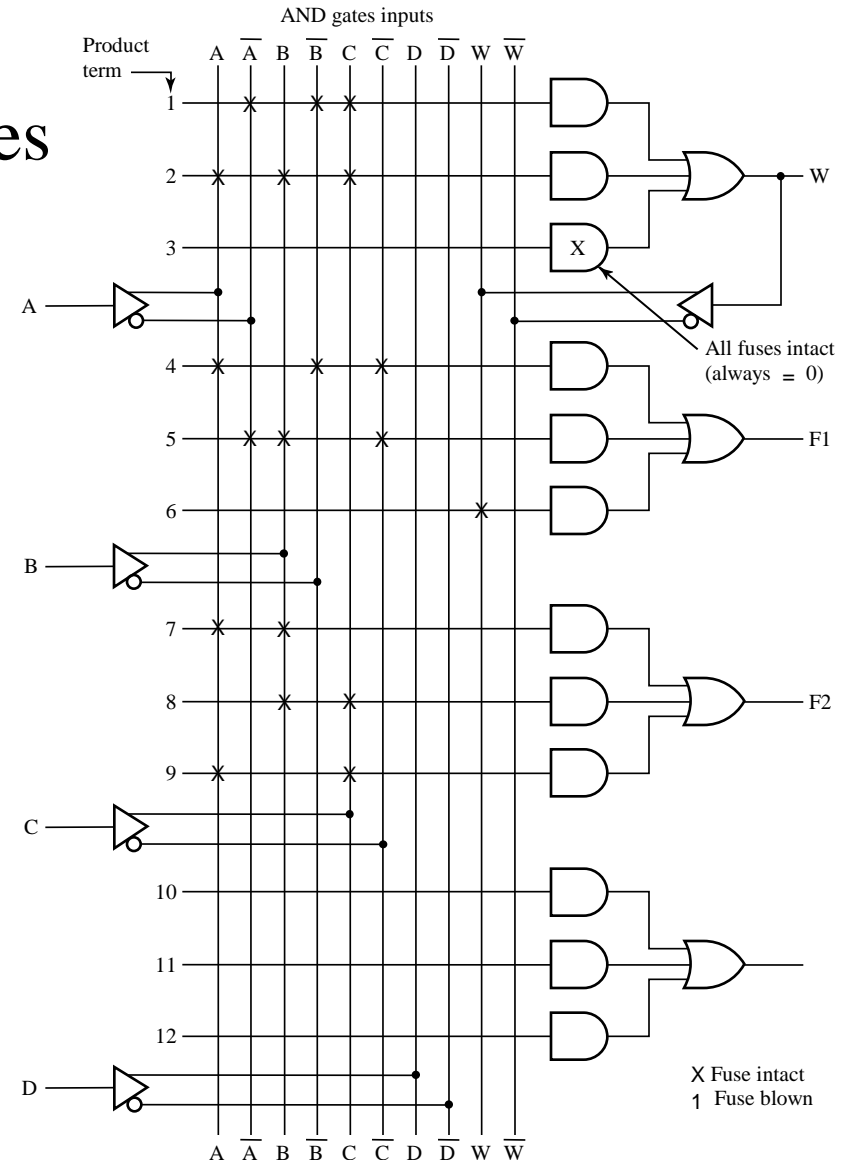

Chapter 5

■ Programmable implementation technologies

• PLA

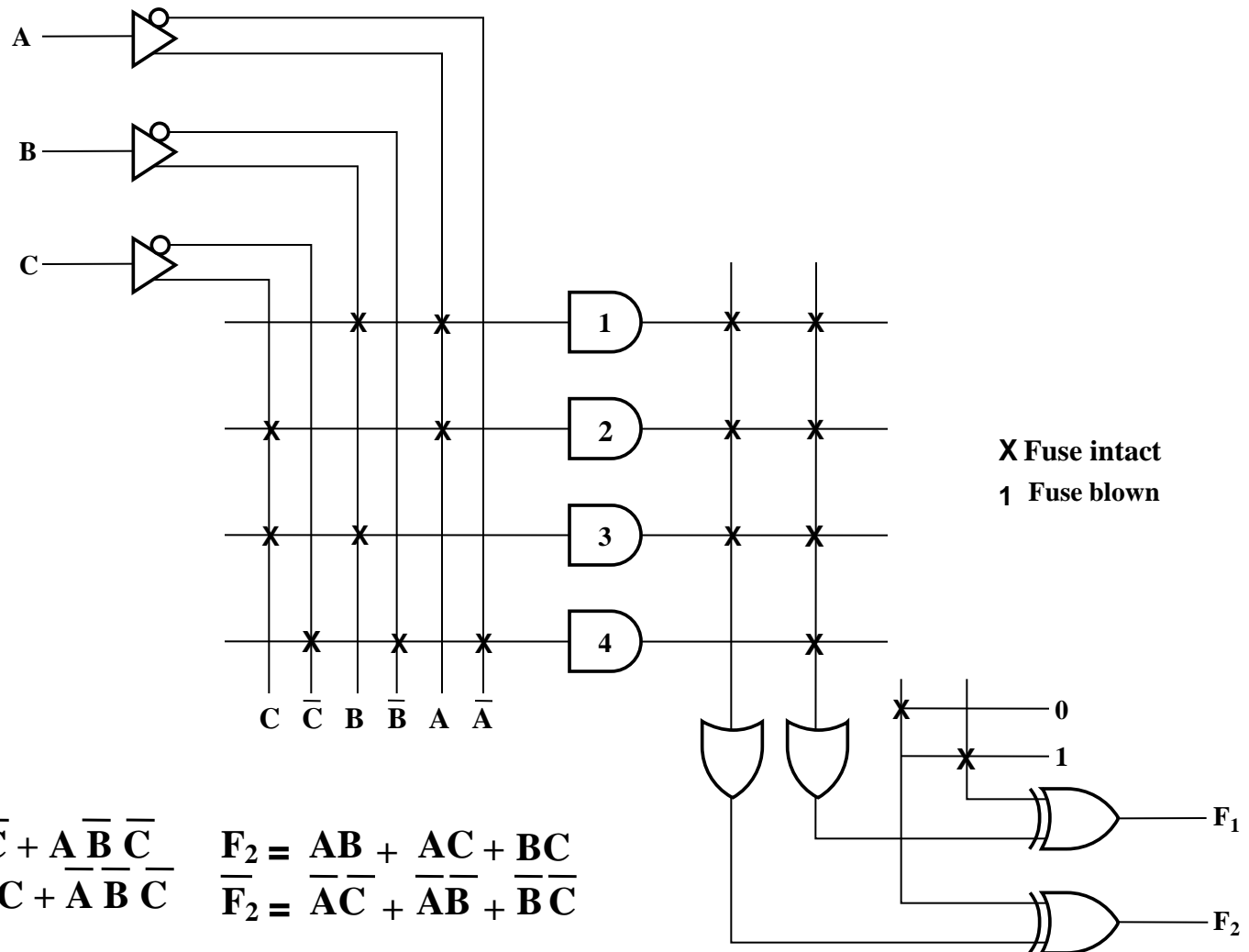


$$\begin{aligned} F_1 &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} \\ \bar{F}_1 &= AB + AC + BC + \bar{A}\bar{B}\bar{C} \end{aligned}$$

$$\begin{aligned} F_2 &= AB + AC + BC \\ \bar{F}_2 &= \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C} \end{aligned}$$


Chapter 5

 - Programmable implementation technologies
 - FPGA
 - Lookup tables (LUTs) are used for implementing FPGAs




Truth table

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

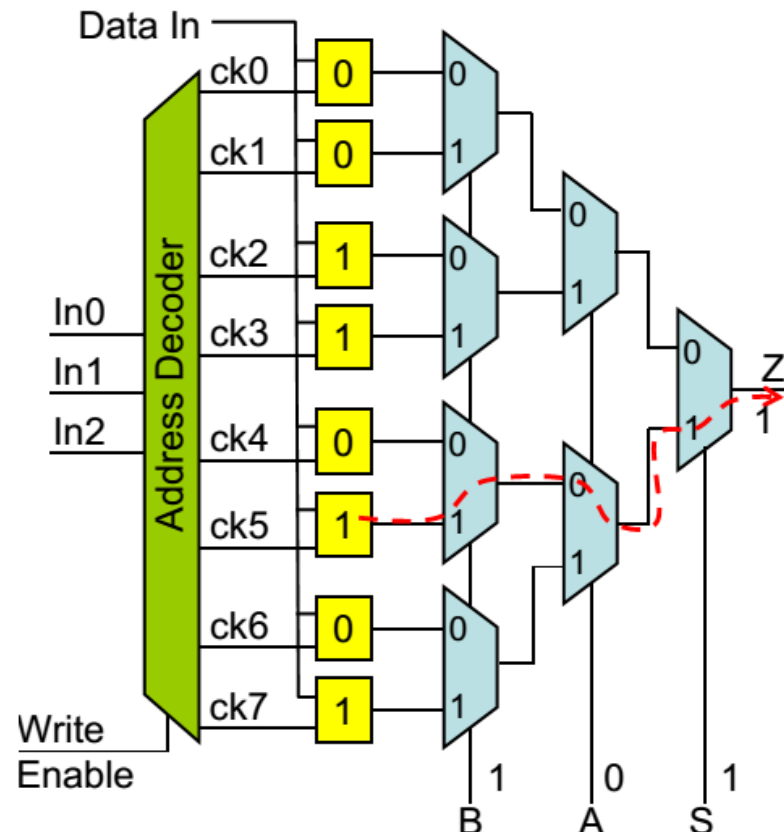

Design of Combinational Circuits

 
- Methods of designing combinational circuits
 - Design by **truth table**
 - Design by **bisection**
 - Design in a **hierarchical structure**
 - Design by **iteration**
 - Design by **contraction/expansion**




Design by **truth table**

Design of Combinational Circuits

■ Design by bisection

 


Decoder expansion

 


Lookup tables

Design of Combinational Circuits

- Design in a hierarchical structure

 


Large shifters using layers of mux

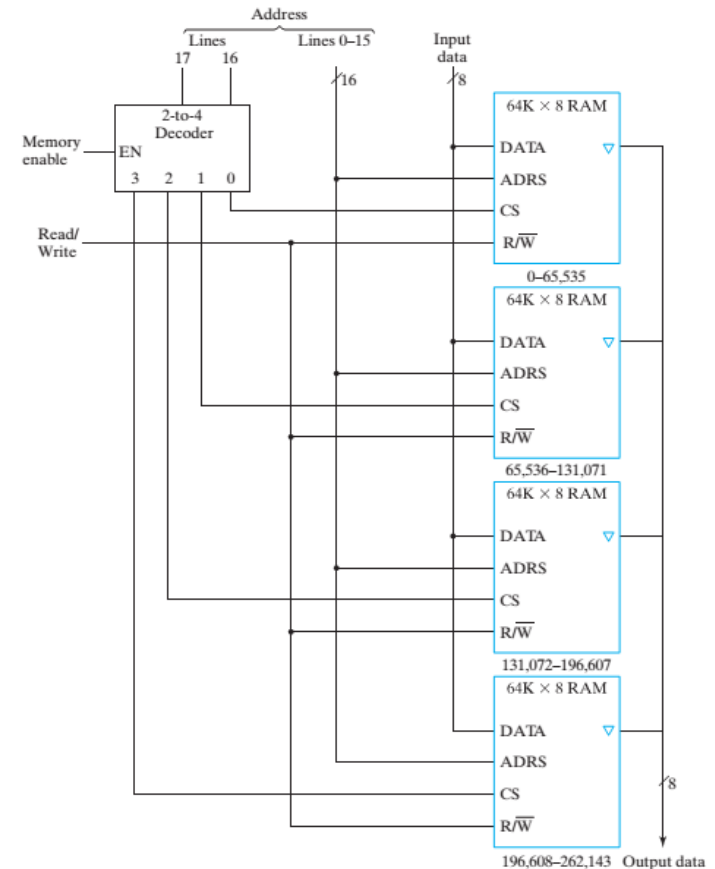

256K * 8 RAM with
four 64K * 8 RAM

Design of Combinational Circuits



- Design by iteration

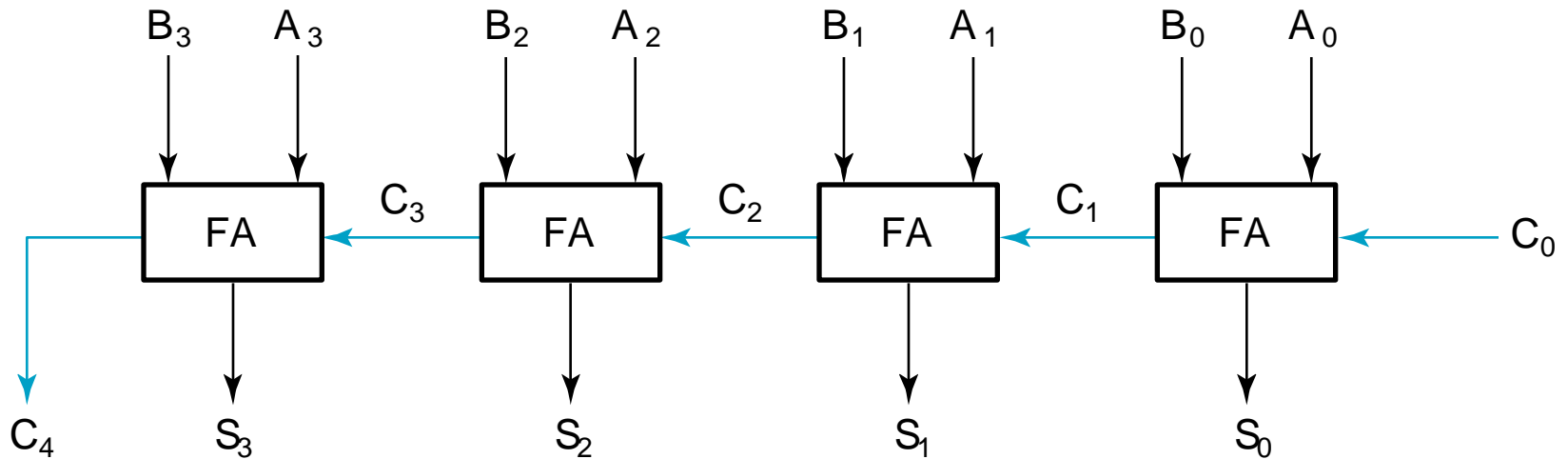


A four-bit Ripple Carry Adder

Design of Combinational Circuits


■ Design by contraction/expansion

  

Contraction of Adder to Incrementer

 

 Expansion of inputs for constructing subtractor



Expansion of inputs for constructing ALU

From classical computing
to quantum computing

From classical computing to quantum computing

Information Representation



classical computing

quantum computing

bit



"0" or "1"
State

  


bit

From classical computing to quantum computing

Information Representation

classical computing

quantum computing

 

superposition





$$\begin{aligned} &|00\rangle \\ &\quad \downarrow \text{quantum gate} \\ &\sqrt{1/2} \cdot |01\rangle + \sqrt{1/2} \cdot |10\rangle \\ &\quad \downarrow \text{quantum gate} \\ &\sqrt{1/2} \cdot |01\rangle + \sqrt{1/6} \cdot |10\rangle + \sqrt{1/3} \cdot |11\rangle \end{aligned}$$

From classical computing to quantum computing

Information Representation

classical computing

quantum computing

    

cross-coupled gates


entanglement

From classical computing to quantum computing


Logic Gate and Logic Operator

classical computing

quantum computing

 

boolean operator

 

unitary operator


From classical computing to quantum computing

Logic Gate and Logic Operator

classical computing


quantum computing

boolean operator

 

unitary operator


- linear transformation
- reversible logic




Inputs		Outputs
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0



XOR gate



input		output	
x	y	x	$y \oplus x$
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

 

Controlled NOT gate


From classical computing to quantum computing

Computational Model



classical computing

quantum computing

sequential computing

 


parallel computing

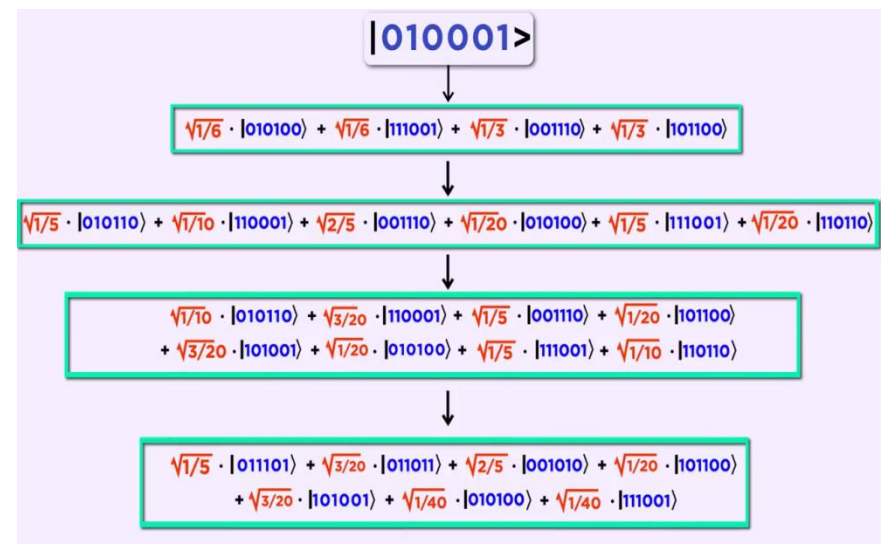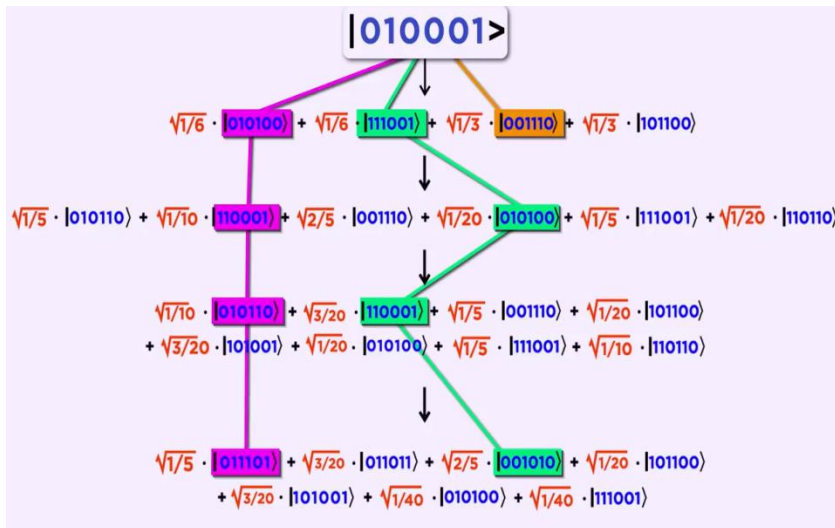

Appendix A: Chapter 3

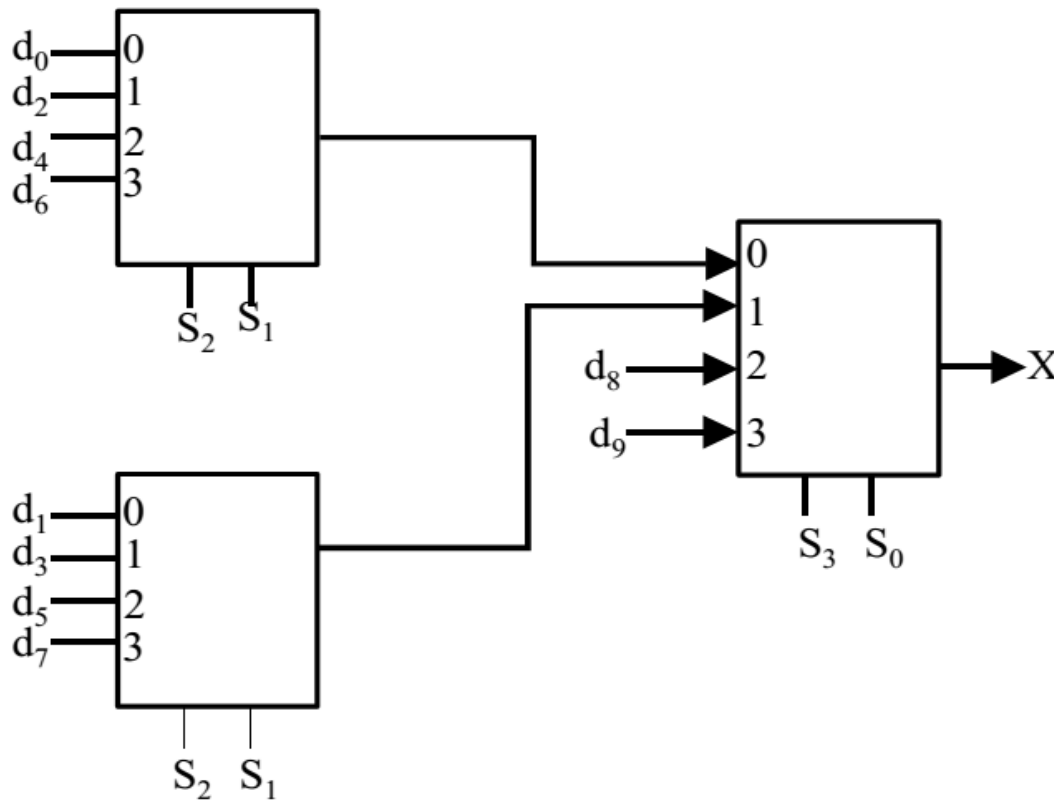
- **Problem:** Construct a 10-to-1 line multiplexer with three 4-to-1 line multiplexers. The selection codes 0000 through 1001 can be directly applied to the multiplexer selections inputs without added logic.



S3	S2	S1	S0	d
0	0	0	0	d0
0	0	0	1	d1
0	0	1	0	d2
0	0	1	1	d3
0	1	0	0	d4
0	1	0	1	d5
0	1	1	0	d6
0	1	1	1	d7
1	0	0	0	d8
1	0	0	1	d9

Appendix B: Chapter 5

- Problem: Given a 256 x 8 ROM chip with **Enable** input, show the external connections necessary to construct a 2K x 8 ROM with eight chips and a decoder.

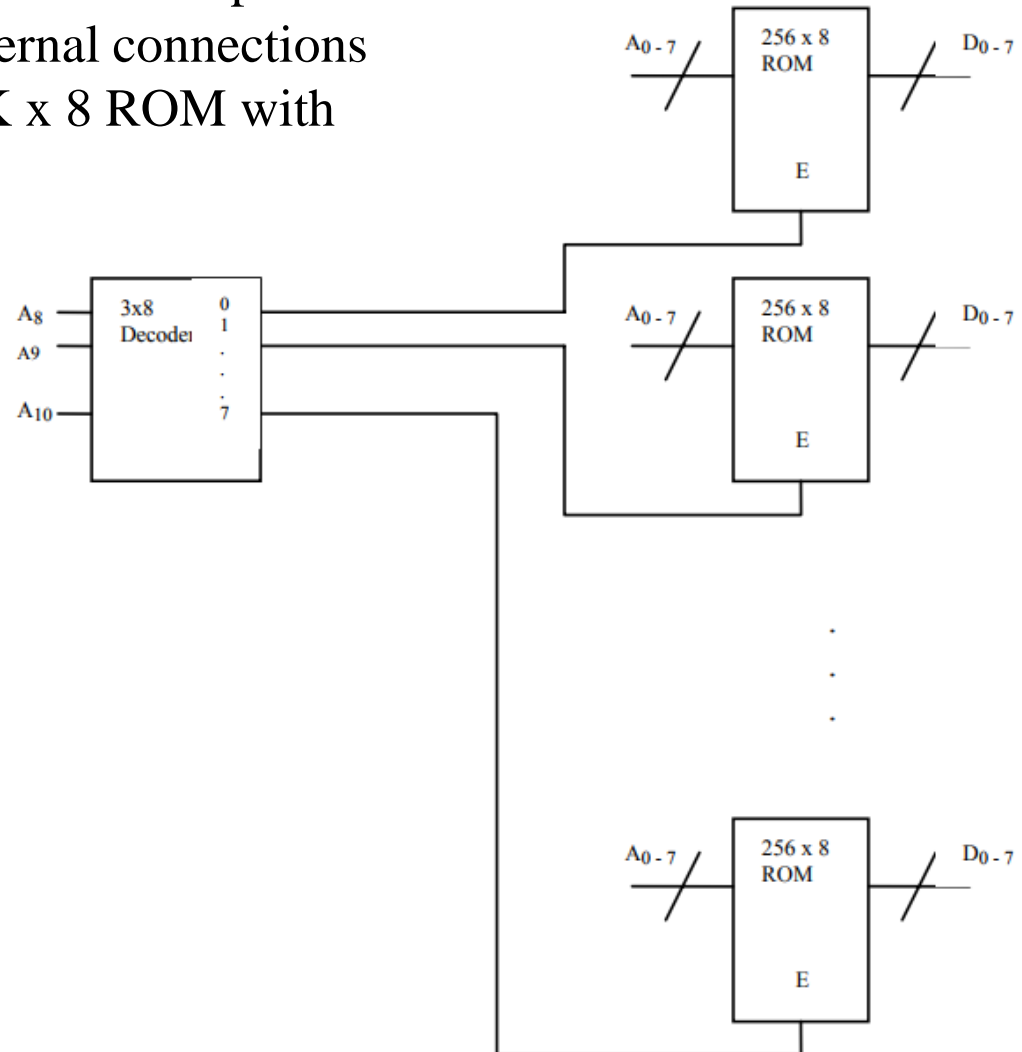

Chapter 5

- Problem: Given a 1K x 4 ROM chip with **Enable** input, show the external connections necessary to construct a 4K x 8 ROM with eight chips and a decoder.

